

DDCO

UNIT-2

CLASS NOTES

feedback/corrections: vibha@pesu.pes.edu

Vibha Masti 


MUXERS, DECODERS & SHIFTERS

MULTIPLEXER — MUX

- multiplexes many inputs into a single output

2:1 MUX


i_0	i_1	j	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

$$y = \bar{j}i_0 + ji_1$$


Symbol

 - Acts as a selector
- if $j=0$, o/p = i_0
if $j=1$, o/p = i_1
- i_0, i_1 : data input
 j : control input



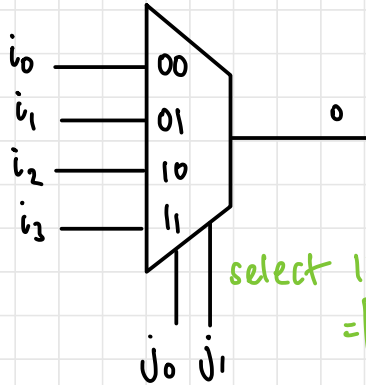4:1 MUX

- Data inputs: i_0, i_1, i_2, i_3
 - Control inputs: j_0, j_1
- 2^n , $n = \text{control}$
 $2^n = \text{data}$




no truth table


($2^6 = 64$ input rows)

select lines
 $= \lceil \log_2(\text{data}) \rceil$ ceil
 
$$o = \bar{j}_1 \bar{j}_0 i_0 + \bar{j}_1 j_0 i_1 + j_1 \bar{j}_0 i_2 + j_1 j_0 i_3$$



4:1 MUX Using 2:1 MUX

 

if $j_1 = 0$, i_0 or i_1
 $j_1 = 1$, i_2 or i_3

n:1 MUX


- for n data inputs, $\lceil \log_2(n) \rceil$ control inputs and one output
- data I/P to be O/P specified by control I/P
- 5-input MUX: $\lceil \log_2 5 \rceil = \lceil 2.322 \rceil = 3$
- n:1 MUX will have $n-1$ 2:1 MUXes

← ceiling

Construct 3:1 MUX using



↳ 2:1 MUX

↳ AND, OR and NOT gates

 

$$o = \bar{j}_0 \bar{j}_1 i_0 + j_0 \bar{j}_1 i_1 + j_1$$

2:1 MUXes

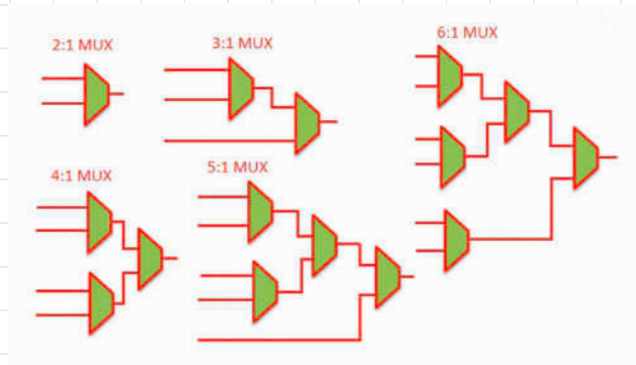 

DECODERS


Floating Value (z) / Tristate Buffer

- for a **third state** (besides 0 and 1)
- in logic circuit, 0 and 1 are **voltage levels**
- binary 0 — 0V, binary 1 — +1.8V (+ve voltage value)
- must be electrically connected to 0V or +1.8V using low resistance path
- what if wire disconnected from both 0V and +1.8V?
High impedance path → electrically disconnected)
- neither 0 or 1; Z (third state)

Tristate Truth Table


e	a	y
0	0	Z
0	1	Z
1	0	0
1	1	1

high impedance state

 

- used in implementation of shared bus
- can be used in MUXes as well

1:2 Decoder

 


inputs: j
outputs: o_0, o_1

$$o_0 = \bar{j}$$
$$o_1 = j$$

if $j=0$,
 $o_0=1, o_1=0$
if $j=1$,
 $o_0=0, o_1=1$

2:4 Decoder

 

$$o_0 = \bar{j}_1 \bar{j}_0$$

$$o_1 = \bar{j}_1 j_0$$


$$o_2 = j_1 \bar{j}_0$$

$$o_3 = j_1 j_0$$

j_1	j_0	o_0	o_1	o_2	o_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

- all o/p's of decoder to be 0
1:4 decoder — not possible

2:3 Decoder

 


$\lceil \log_2 n \rceil : n$ decoder

- n data outputs
- $\lceil \log_2 n \rceil$ control inputs ← ceiling


2:1 MUX Using Tristate Buffers

- 2 tristate buffers, 1 inverter

 

4:1 MUX

- 2:4 decoder, 4 tristate buffers

 

Applications of Decoders

eg: full subtractor $f(x, y, z)$


$$D = \sum(1, 2, 4, 7)$$

$$B = \sum(1, 2, 3, 7)$$

$$0 - 1 - 0 = 1 \quad 1$$

decoder outputs are minterms

connect minterms

 


full subtractor


a	b	C-bin	d	b _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 Question 1

Construct 7-segment display using decoder




a	b	c	d	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	1	0	1	0	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	1	0	1	1	9

 

Shifters

Left Shift

Left shift 8-bit no. by 1

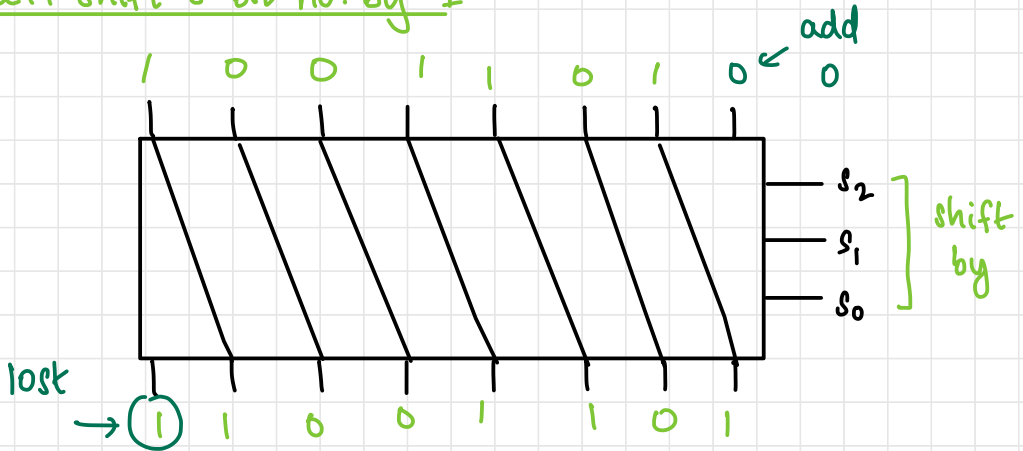

- max number of positions to left-shift = 7
- left shifting by 8 or greater: 0 (meaningless)


Bit	0	1
s_2	shift by 0	shift by 4
s_1	shift by 0	shift by 2
s_0	shift by 0	shift by 1

] total will be cumulative

eg: $s_2 s_1 s_0 = 111 \Rightarrow$ total shift is $4+2+1 = 7$ shifts
 $s_2 s_1 s_0 = 101 \Rightarrow$ total shift is $4+0+1 = 5$ shifts

All three bits are independent of the other shifts

Barrel Shifter Structure

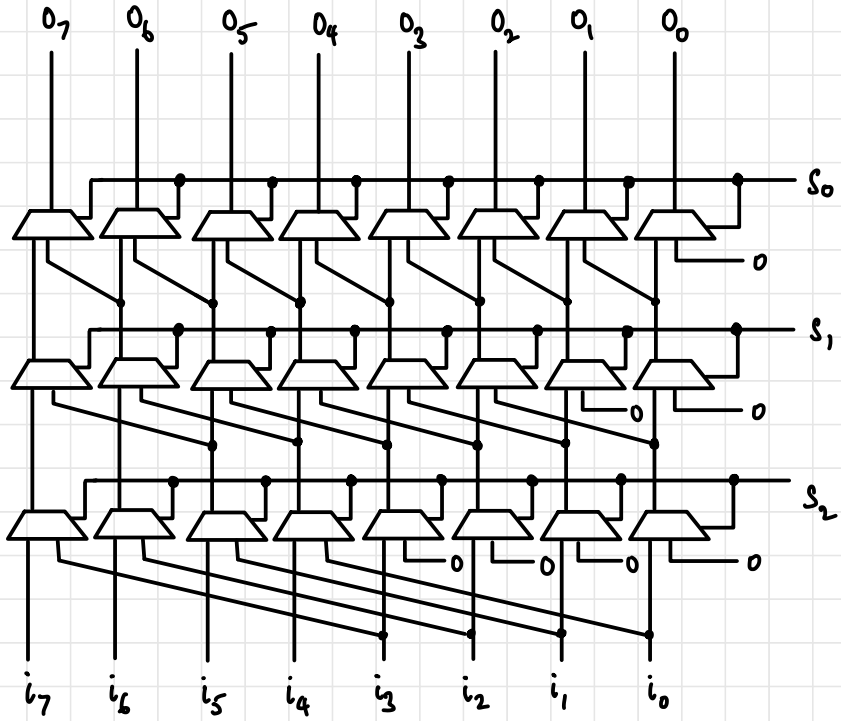


DELAYS

Propagation Delay

Time taken for change in I/P to reflect in O/P.

1) Gate


Timing diagram

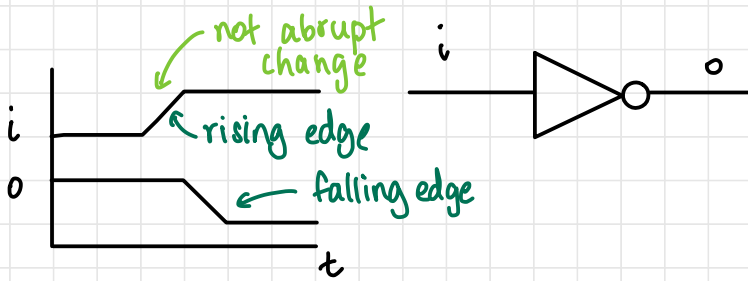


2) Logic circuit

- critical path: path whose delay takes the longest
- assume $t_{pd} = 100 \text{ ps}$ ← propagation delay
- delay due to change in any input → depends on no. of gates

Example: MUX Circuit

 

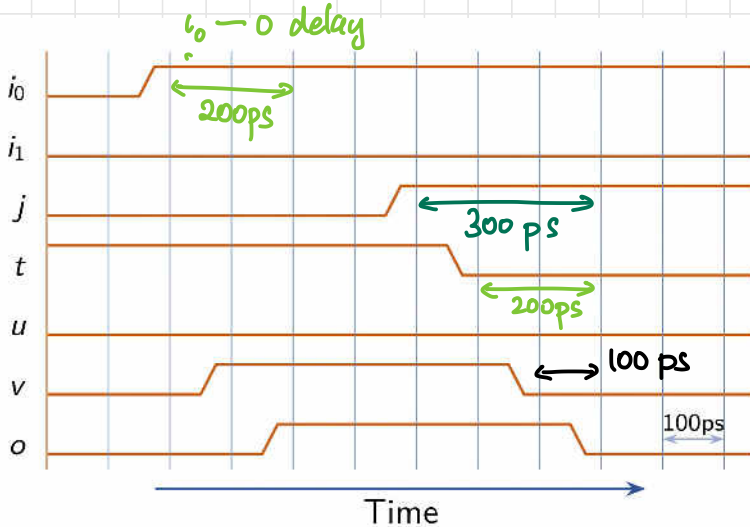- change in i_0 : 2 gates = 200ps
- change in i_1 : 2 gates = 200ps
- change in j : 3 gates = 300ps ← critical path delay




Critical path delay of MUX circuit = 300ps

How many 1/P changes per second?

$$1 \div (300 \times 10^{-12}) = 3.33 \text{ GHz}$$


Question 2

What A: $1 \rightarrow 0$, delay = 100ps

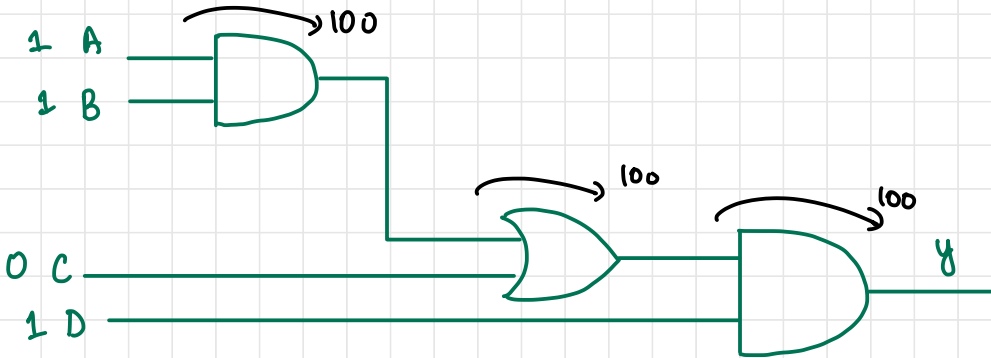

critical delay = 300ps


Question 3

 

o/p: $1 \rightarrow 0 \rightarrow 1 \leftarrow$ stable


Question 4

Construct 4:16 decoder with five 2:4 line decoders with enable input

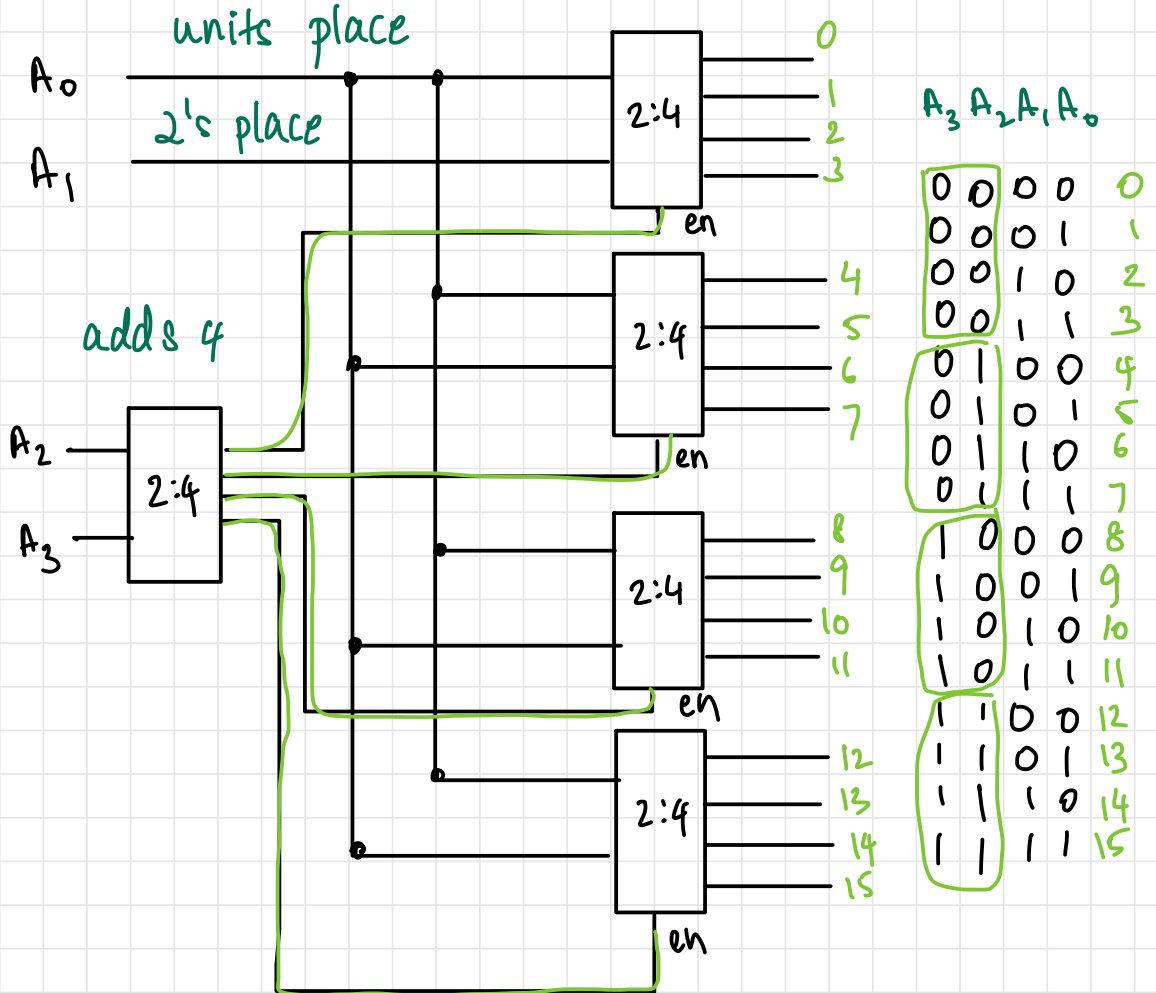

Question 5

Construct 4:16 decoder with two 3:8 decoders and a not gate

 


Question 6


Full adder using MUX

$$s(x, y, z) = \sum(1, 2, 4, 7)$$

$$c(x, y, z) = \sum(3, 5, 6, 7)$$

 

x	y	z	s	c
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


SEQUENTIAL LOGIC CIRCUITS

- Logic circuits that have memory/ storage elements (state of logic circuit)
- Output fed back to input

Simplest Memory Unit

Single inverter

 


$$\begin{aligned} \text{Assume } o/p = 0 &\Rightarrow i/p = 1 \\ o/p = 1 &\Rightarrow i/p = 0 \end{aligned}$$

impossible!!

astable output

- does not work


Two inverters

 

stable!!

SR Latch (Set-Reset Latch)

- Cross-coupled NOR gates

 


stable, but to be avoided (forbidden)

Truth table

s	r	q	\bar{q}
0	0	q_{prev}	\bar{q}_{prev}
0	1	0	1
1	0	1	0
1	1	0	0

memory

also drawn like

 


for $s=0, r=0$


Case 1: $q = D$
 $\therefore q = 1$
 $q = 0$

Case 2: $q = \bar{D}$
 $q = 0$
 $q = 1$

retains previous values

 

NAND-Based SR Latch

 


Truth table

\bar{s}	\bar{r}	q	\bar{q}
0	0	q_{prev}	\bar{q}_{prev}
0	1	1	0
1	0	0	1
1	1		

forbidden

D Latch (Data)

 


clk	d	s	r	q	\bar{q}
0	0	0	0	q_{prev}	\bar{q}_{prev}
0	1	0	0	q_{prev}	\bar{q}_{prev}
1	0	0	1	0	1
1	1	1	0	1	0

memory

transparent

 - no indeterminate states
- level sensitive - changes when $clk = 1$



Level sensitive

↳ +ve level sensitive

↳ -ve level sensitive


Edge sensitive

↳ rising edge trigger



↳ falling edge trigger

D-Flip Flop

- Edge triggered- flip flops

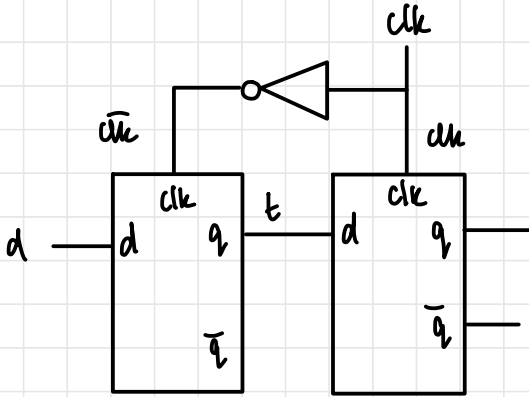


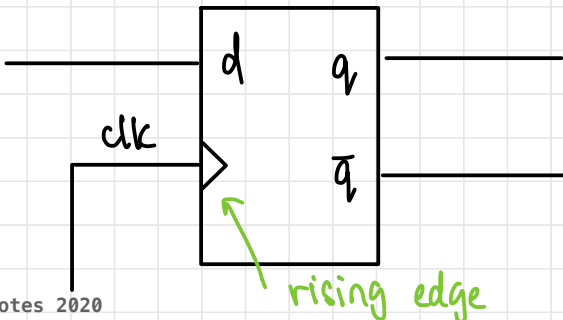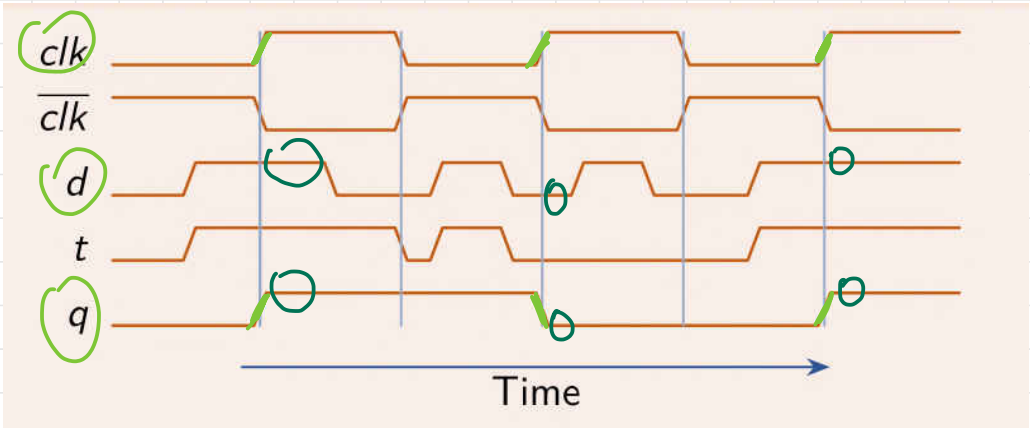- When \overline{clk} is 1, t reflects d
- when clk is 1, changes in d are ignored and prev t value is retained




J-K Flip Flop

j	k	q	\bar{q}
0	0	q_{prev}	$\overline{q_{\text{prev}}}$
0	1	0	1
1	0	1	0
1	1	$\overline{q_{\text{prev}}}$	q_{prev}

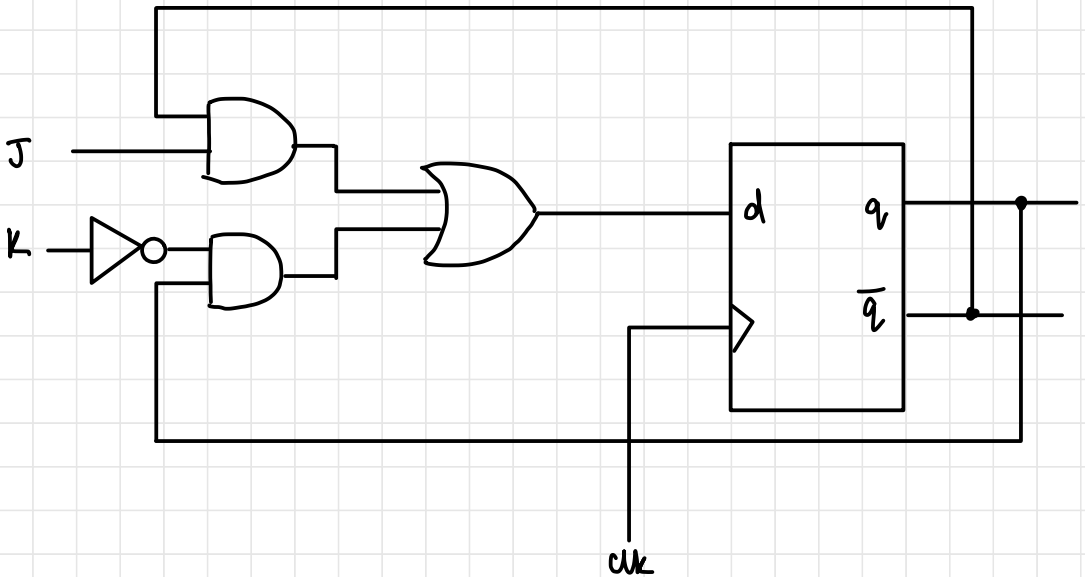


4-Bit Shift register

8150

 


Input: 1010


①

 


②

 

③

 


④

 


8-Bit Shift Register

PIPO (parallel in, parallel out)

 


Symbol

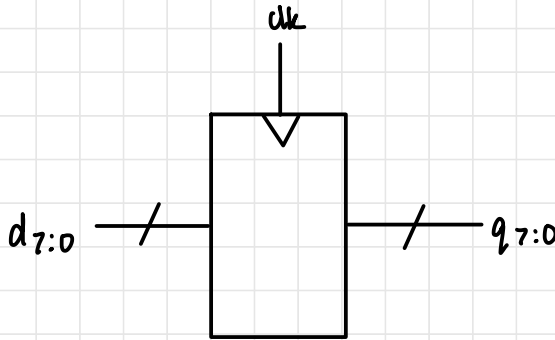


Flip Flop with Enable

1) Clock Gating Approach

 


- clk signal is gated
- can cause timing problems
- careful use can reduce power consumption - useful here
- usually avoided

2) MUX

 

Symbol

 


- At rising edge of clock

en	d	q
0	0	q_{prev}
0	1	q_{prev}
1	0	0
1	1	1


Resettable Flip Flop

 - When $reset = 0$, d-flip flop normal
- When $reset = 1$, d-flip flop stores 0
- Force memory elements into known state
- Initial power supply — prevent randomness



Construct JK Flip Flop Using enable/reset

Flip Flop with Enable

 


J-k flip-flop truth table

j	k	q	\bar{q}
0	0	q_{prev}	$\overline{q_{\text{prev}}}$
0	1	0	1
1	0	1	0
1	1	$\overline{q_{\text{prev}}}$	q_{prev}

Synchronous Sequential Logic Circuits


2) Loops

- inverter loop is a problem

 

unstable


- solution: insert flip flop

 


stable: toggles at every clock rising edge

 1) Race Condition


- Memory elements can suffer from race conditions (race hazards)
- depends on relative timing of clks
- if clk_1 arrives before clk_2 , race condition



- solution: common clock synchronisation

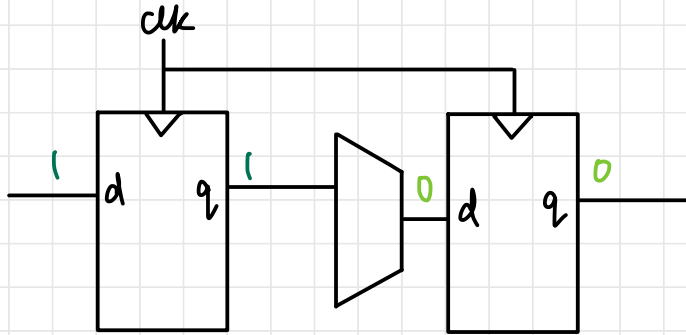

 - if clk time period is greater than critical path delay race condition eliminated



Synchronous Sequential Logic Circuit


- 1) Every circuit element is either a register (flip flop) or a combinational circuit
 - ↳ no latches alone, only flip flops
 - ↳ think of flip flops as indivisible units
- 2) At least one circuit element is a register
- 3) All registers receive same clock signal
- 4) Every cyclic path has at least one register
 - ↳ no inverter loops

Classify the following logic circuits as combinational or synchronous sequential or neither

- ▶ AND gate (output not connected to own input) **combinational logic circuit**
- ▶ AND gate (output connected to own input) **neither**
- ▶ D flip-flop **synchronous sequential logic circuit**
- ▶ SR latch **neither**
- ▶ Series of D flip-flops (with common clock) with output of one connected to the input of the next via an inverter **synchronous sequential logic circuit**



FINITE STATE MACHINES

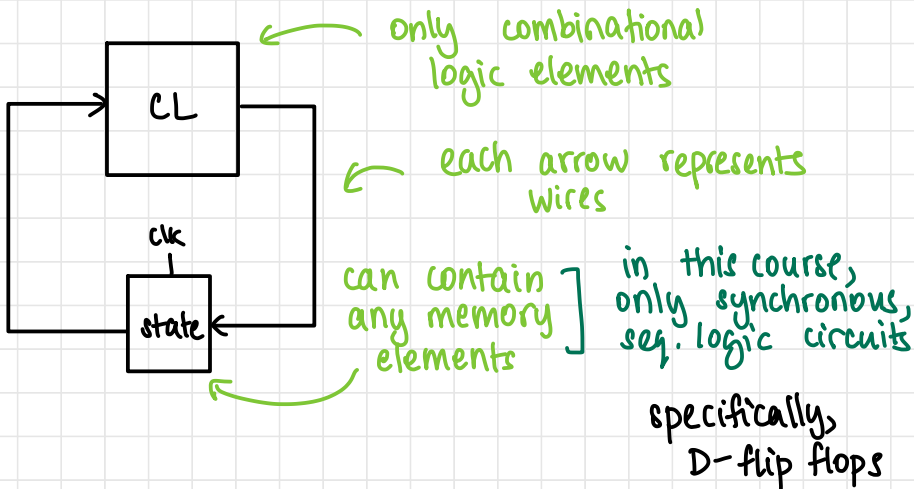- Mathematical foundation for sequential logic circuits
- Consists of two blocks - CL and state block





- Any sequential logic circuit (from a counter to a complex microprocessor) can be represented as an FSM
- Fundamental concept in CSE
- In AFLL, nodes and edges, but to implement, this

  - This diagram lacks input & output
- Two types – Mealy type and Moore type FSMs
- Four input/output possibilities




  - if I/P given to state block, delayed by one clock cycle and therefore neglected




Mealy FSM

 - o/p depends on current state as well as input




Moore FSM

- Output depends only on current state

 

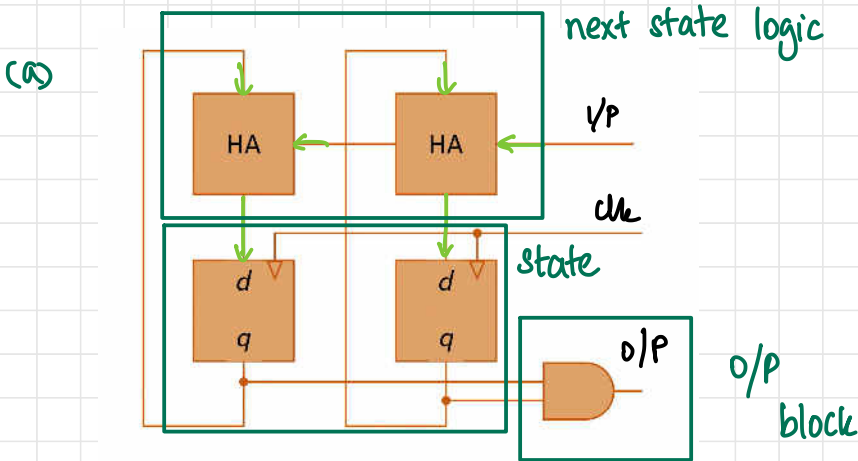
Question 7

Identify as Mealy or Moore & make into blocks



Moore FSM

(b)

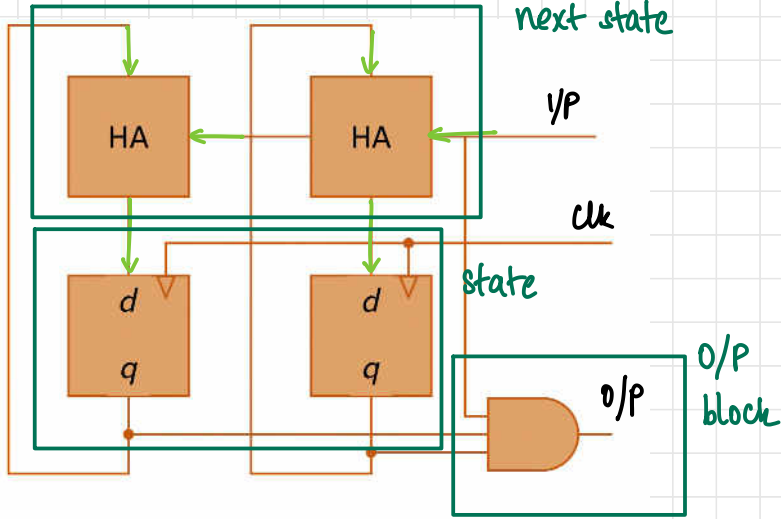

Mealy FSM

Designing an FSM (Moore)

1. Determine input/output
2. State transition diagram
 - ↳ no. of states
 - ↳ draw diagram
3. Encoding tables
 - ↳ state d-flip flops
 - ↳ output
4. State transition table
5. Output table } ~ truth tables
6. Logic minimisation
 - ↳ Boolean formulas
7. Logic circuit construction

Question 8

Lift/elevator control logic (2 floors)

Inputs


- Lift has a switch which can be in the down or up position, indicating that the lift should go down or up respectively
- The switch signal switch-up is 0 when lift should go down and is 1 when the lift should go up
- Lift system has a sensor which indicates when the lift is stationary or moving between floors.
- Signal on-floor is 1 when lift is at ground or first floor and is 0 when in between

Outputs

- Signal lift-up when lift should move up
- Signal lift-down when lift should move down
- Signal on-ground is 1 when on ground floor and 0 when on first floor
- Signal on-first is 1 when on first floor and 0 when on ground floor


Reset/start state

- Elevator initially on ground floor.

 

State Transition Diagram

 - Visual FSM
- states/ nodes/ vertices \rightarrow circles
- Transition between states \rightarrow line segments/ arrows/ arcs/ edges
- Each contains Boolean formula of inputs as label
- Determine no. of states (2 in transition, 2 stationary)



State Encoding Table

State	Encoding (s_1, s_0)
f_0	00
f_{01}	01
f_1	11
f_{10}	10

State	Encoding (s_1, s_0)
f_0	00
f_{01}	01
f_1	11
f_{10}	10

Output Encoding Tables

- on-ground

Meaning	Encoding
Lift on ground floor	1
Lift anywhere else	0

- on-first

Meaning	Encoding
Lift on first floor	1
Lift anywhere else	0

- lift-up


Meaning	Encoding
Lift going from ground to first floor	1
Lift anywhere else	0

- lift-down

Meaning	Encoding
Lift going from first to ground floor	1
Lift anywhere else	0

State Transition Table

		Current State		Inputs		Next State	
		s_1	s_0	switch_up	on_floor	s'_1	s'_0
f_0	[0	0	0	no change	0	0
		0	0	0		1	0
		0	0	1	go to f_{01}	0	0
		0	0	1		1	0
f_{01}	[0	1	0		0	1
		0	1	0		1	1
		0	1	1		0	1
		0	1	1		1	1
f_{10}	[1	0	0		0	no change
		1	0	0	go to f_0	1	0
		1	0	1		0	1
		1	0	1		1	0
f_1	[1	1	0	go to f_{10}	0	1
		1	1	0		1	0
		1	1	1	no change	0	1
		1	1	1	no change	1	1

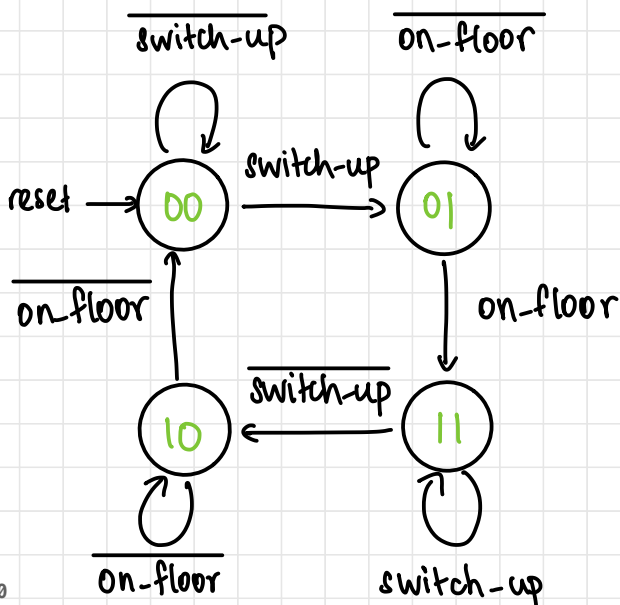

Output Table

State		Outputs				
		s_1	s_0	on_ground	on_first	lift_up
on floor	0	0	1	0	0	0
	0	1	0	0	1	0
in trans.	1	0	0	0	0	1
	1	1	0	1	0	0

K-map for s_1'

		switch_up on_floor			
		00	01	11	10
$s_1 s_0$	$\bar{s}_1 \bar{s}_0$ 00	0	0	0	0
	$\bar{s}_1 s_0$ 01	0	1	1	0
	$s_1 s_0$ 11	1	1	1	1
	$s_1 \bar{s}_0$ 10	1	0	0	1

$$s_1' = \overline{\text{on_floor} \cdot s_1} + s_0 \cdot \overline{\text{on_floor}}$$

K-map for s_0'

		switch_up on_floor			
		00	01	11	10
$s_1 s_0$	$\bar{s}_1 \bar{s}_0$ 00	0	0	1	1
	$\bar{s}_1 s_0$ 01	1	1	1	1
	$s_1 s_0$ 11	0	0	1	1
	$s_1 \bar{s}_0$ 10	0	0	0	0

$$s_0' = \bar{s}_1 s_0 + \text{switch_up} \cdot \bar{s}_1 + \text{switch_up} \cdot s_0$$

Boolean Formulas

Next state

$$s_1' = \overline{\text{on_floor}} \cdot s_1 + s_0 \cdot \overline{\text{on_floor}}$$

$$s_0' = \overline{s_1} \cdot s_0 + \text{switch_up} \cdot \overline{s_1} + \text{switch_up} \cdot s_0$$

Outputs


$$\text{on_ground} = \overline{s_1} \cdot \overline{s_0}$$

$$\text{on_first} = s_1 \cdot s_0$$

$$\text{lift_up} = \overline{s_1} \cdot s_0$$

$$\text{lift_down} = s_1 \cdot \overline{s_0}$$


Logic Circuit

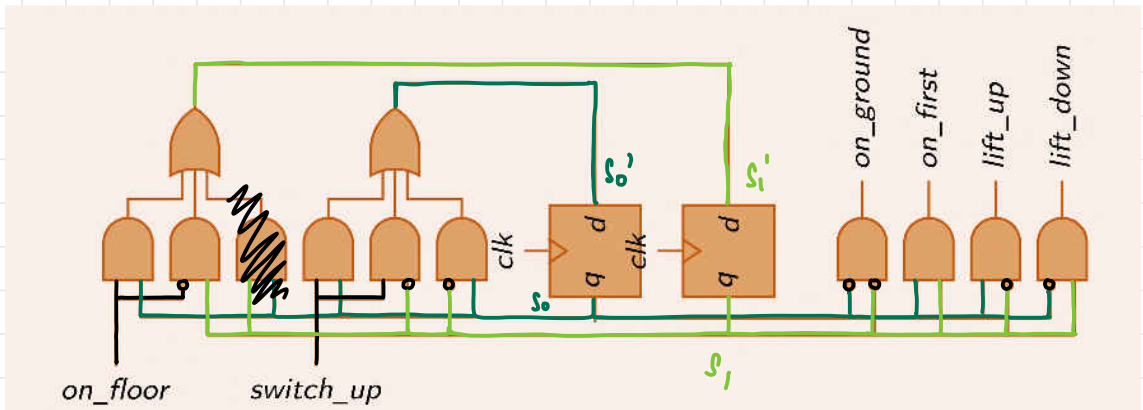

Moore FSM


State table for Moore Machine

Present state	Next state		Output
	Input		
	I_1	I_2	
A	A	B	O_1
B	D	A	O_2
C	B	D	O_1
D	A	C	O_2

 

Mealy Machine


Present state	Next state, output	
	Input	
	I_1	I_2
A	A, O_1	B, O_1
B	D, O_2	A, O_2
C	B, O_1	D, O_1
D	A, O_2	C, O_2

 

Question 9


Elevator Problem as a Mealy Machine

- depends on Y/P

 

- Determine no. of states — here only 2 states
- state f_0 : lift on ground floor or in transit to ground floor
- state f_1 : lift on first floor or in transit to first floor

← O/P signal asserted

 

State Encoding Table

State	Encoding (s, s ₀)
f_0	0
f_0	1

Output Encoding Tables

- on-ground

Meaning	Encoding
Lift on ground floor	1
Lift anywhere else	0

- on-first

Meaning	Encoding
Lift on first floor	1
Lift anywhere else	0

- lift-up


Meaning	Encoding
Lift going from ground to first floor	1
Lift anywhere else	0

- lift-down

Meaning	Encoding
Lift going from first to ground floor	1
Lift anywhere else	0

State Transition & Output Table - Mealy

Current State	Inputs		Next State	Outputs			
	s	s'		on_ground	on_first	lift_up	lift_down
f_0	0	0	0	0	0	0	1
	not on gnd	doesn't matter	stays	not yet	no	no	yes
f_0	0	1	0	1	0	0	0
	on gnd	stay	stays	on gnd	no	no	no
f_0	0	1	1	0	0	1	0
	on gnd	go up	move	no	no	yes	no
f_1	1	0	1	0	0	1	0
	not on first	doesn't matter	stays	no	not yet	yes	no
f_1	1	1	0	0	0	0	1
	on first	go down	move	no	no	no	yes
f_1	1	1	1	0	1	0	0
	on first	stay	stays	no	yes	no	no

 

K-maps

K-map for s'

		on_floor switch_up			
		00	01	11	10
s	0	0	0	1	0
	1	1	1	1	0

$$s' = \overline{\text{on_floor}} \cdot s + \text{on_floor} \cdot \text{switch_up}$$

$$\text{on-ground} = \bar{s} \cdot \text{on_floor} \cdot \overline{\text{switch_up}}$$

$$\text{on-first} = s \cdot \text{on_floor} \cdot \text{switch_up}$$

K-map for lift-up

		on_floor switch_up			
		00	01	11	10
s	0	0	0	1	0
	1	1	1	0	0


$$\text{lift-up} = s \cdot \overline{\text{on_floor}} + \bar{s} \cdot \text{on_floor} \cdot \text{switch_up}$$

K-map for lift-down

		on_floor switch_up			
		00	01	11	10
s	0	1	1	0	0
	1	0	0	0	1

$$\text{lift-down} = \overline{\text{on_floor}} \cdot s + \text{on_floor} \cdot \overline{\text{switch_up}} \cdot s$$

Logic Circuit

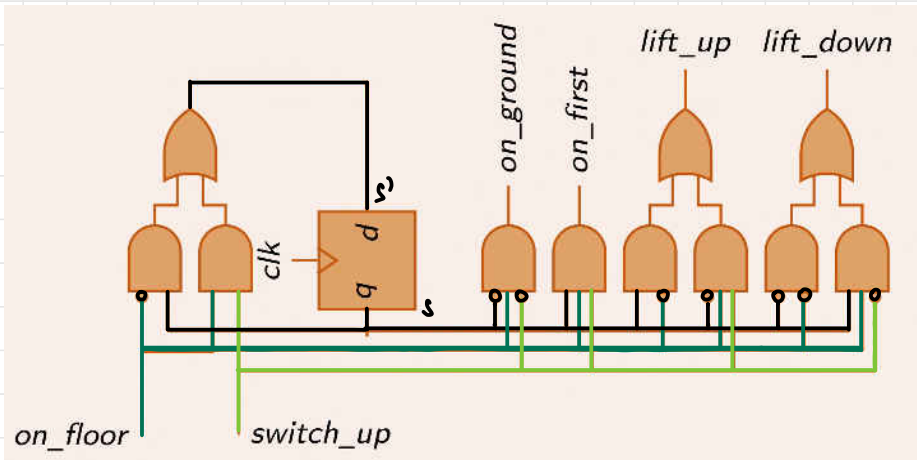


Mealy FSM

Revision Questions

Q1. Implement NOT, AND and OR using 2:1 MUX


NOT

x	f
0	1
1	0

 


AND

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

 

OR

x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

 


Q2. Construct 2:1 Mux using only 2-input NAND gates. How many gates are required?

selection	Output
0	i_0
1	i_1

$$y = \bar{s}i_0 + si_1$$
 
$$= \overline{(\bar{s}i_0 \cdot (si_1))}$$



Q3. Implement a decoder for the equation $f(x,y,z) = \sum(1,2,4,7)$

